



waag society

institute for art, science and technology




BioHack Academy Incubator Design

Picture by Bas Uterwijk



What it means to be a hacker

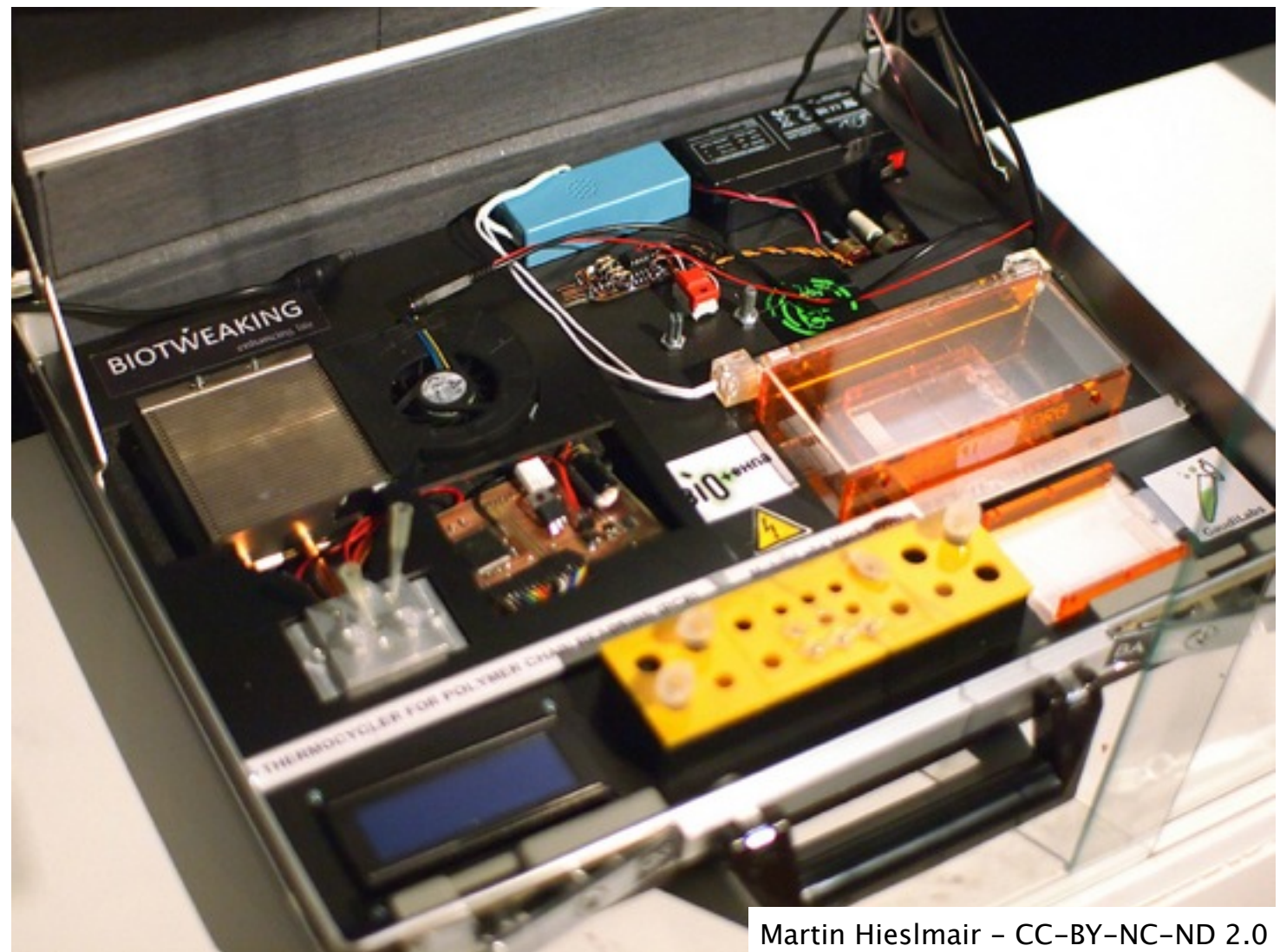- Create & Share
- Freedom of inquiry
- Hostility of secrecy
- Sharing as ideology and strategy
- The right to fork
- Emphasis on rationality
- Distaste of authority
- Playful cleverness






Why we need an incubator

- Microbes like a certain temperature
- Temperature dependent:
 - Enzyme reactions
 - DNA interactions
 - Cell state





Industry standard

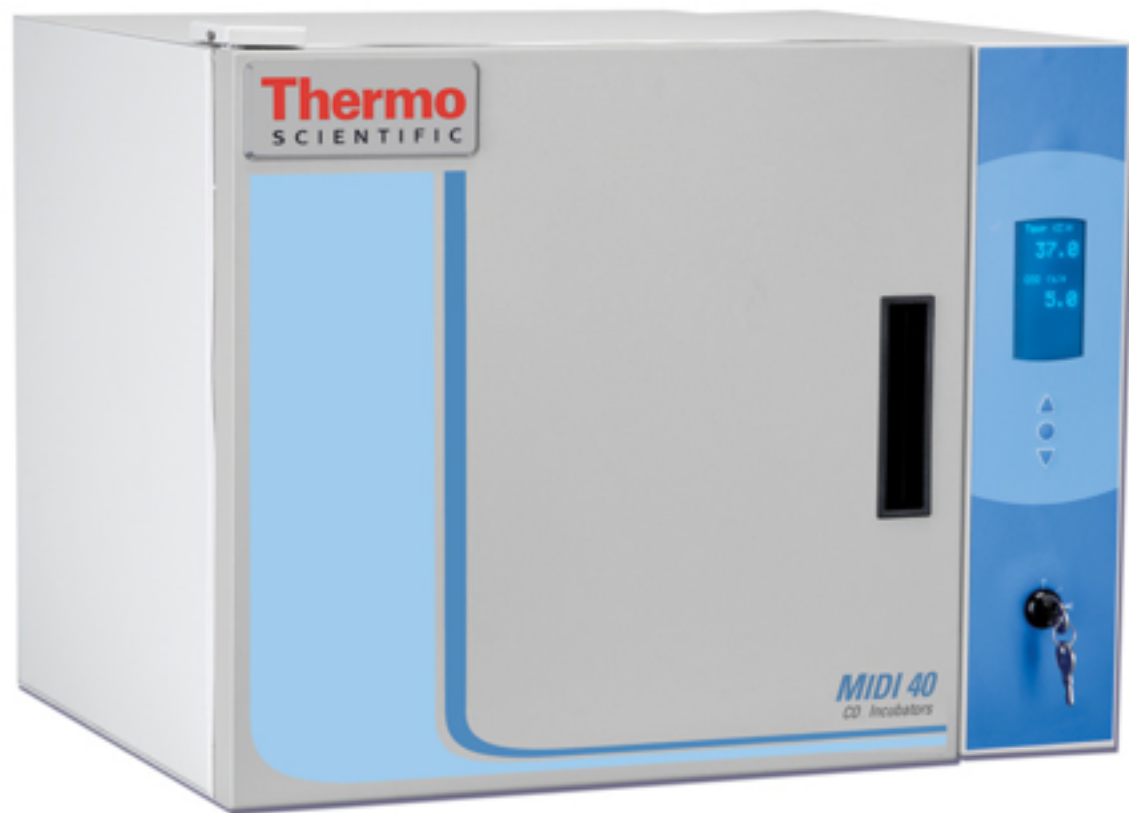



Function

- Heat isolated enclosed cabinet, with see-through window
- Heat source
- Temperature controller
- Temperature indicator
- User interface to set temperature

<http://biohackacademy.github.io/biofactory/class/1-incubator/requirements/>



Design constraints:


- 9 cm petri dishes





The Biohack Academy design
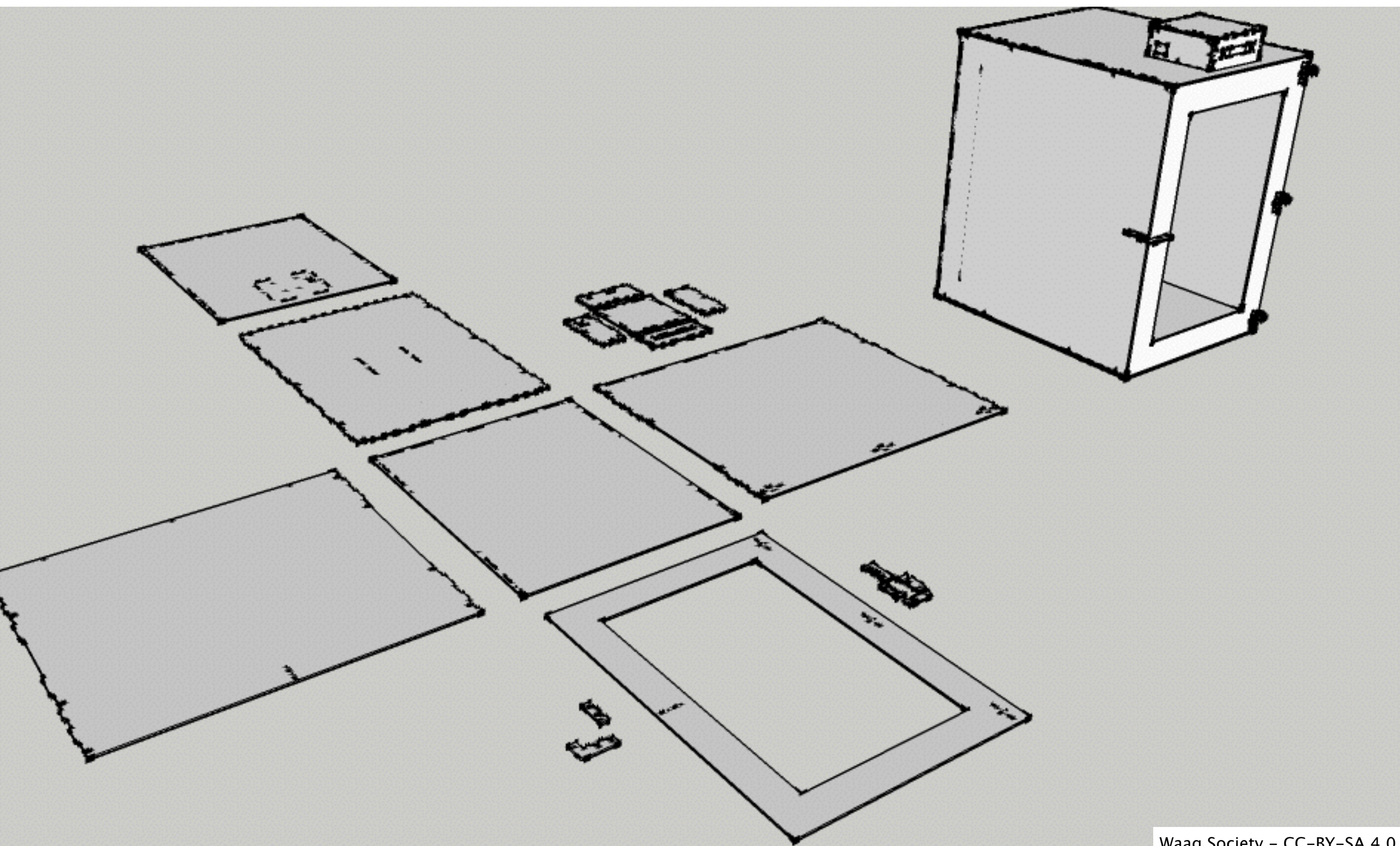
<http://biohackacademy.github.io/biofactory/class/1/Incubator-Sketchup.skp>





Bill of Materials

#	Amount	Description	Function
1	1	3mm MDF	Outer structure
2	1	Expanded polystyrene (EPS) 5 plates of 100 x 50 x 5cm	Insulation
4	1	3mm Acrylic sheet 25 x 35 cm	Window
5	1	100W infrared light bulb, fitting and power cord	Heating
6	1	12V 80 mm Axial Fan	Air distribution inside incubator
7	1	Light switch	Switch incubator on/off
8	1	Water proof temperature sensor	Measure inside temperature
9	1	4 section 7 segment display	Display temperature
10	1	MOSFET	Control fan speed
11	4	10K resistor	Pull up for buttons, thermistor and mosfet
12	1	Diode	Part of MOSFET circuit
13	2	Buttons	User interaction panel
14	1	White LED	Light inside incubator
15	1	220 Ohm resistor	LED resistor
16	1	7.5 W power supply	Powering the Arduino and Fan
17	1	Jack Adapter	Power connector
18	1	Relay	Controlling the 100W light bulb




Powering an LED





LED circuit

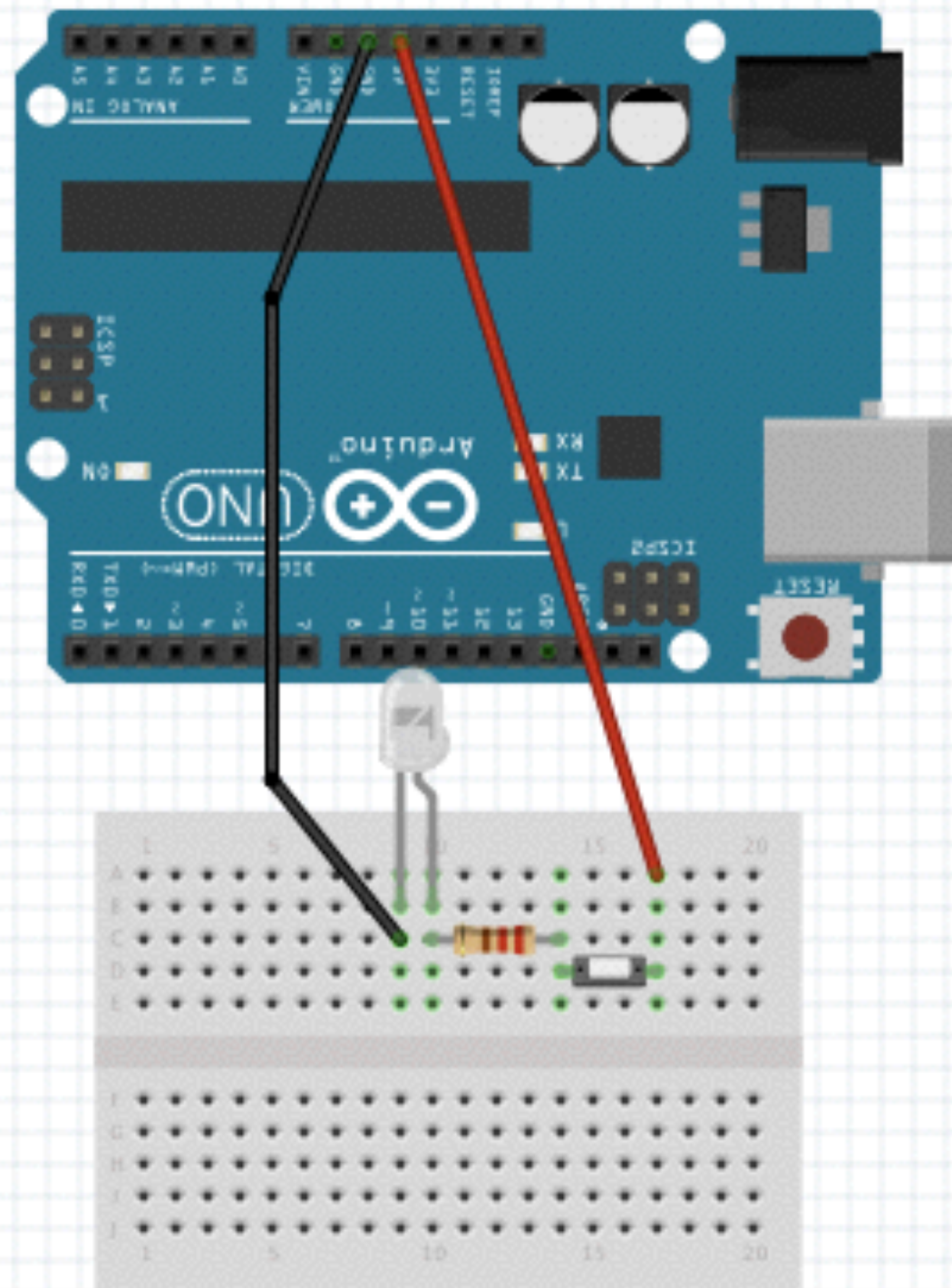




Sensing the temperature

- 10K thermistor






Sensing the temperature

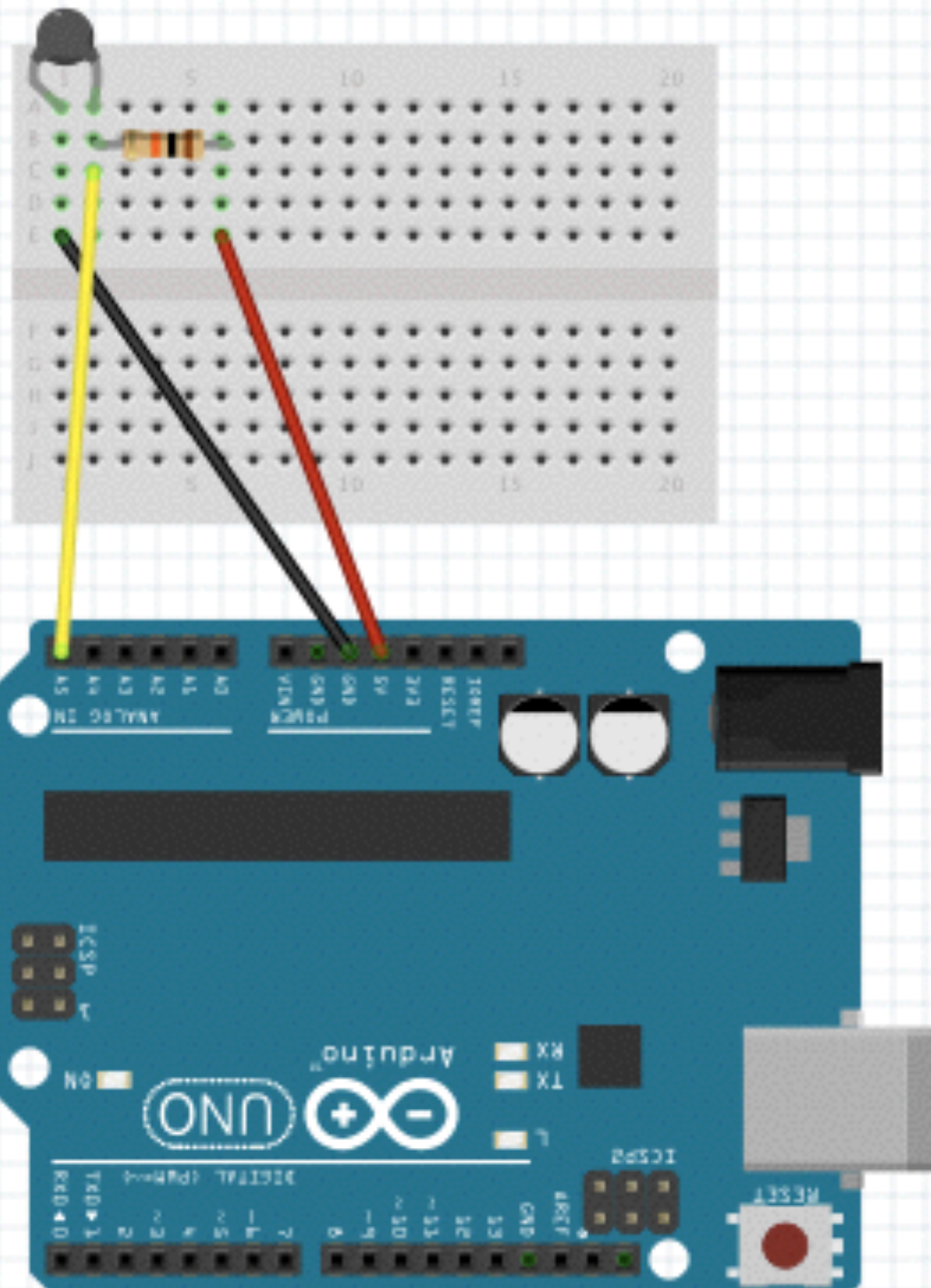



Schematic
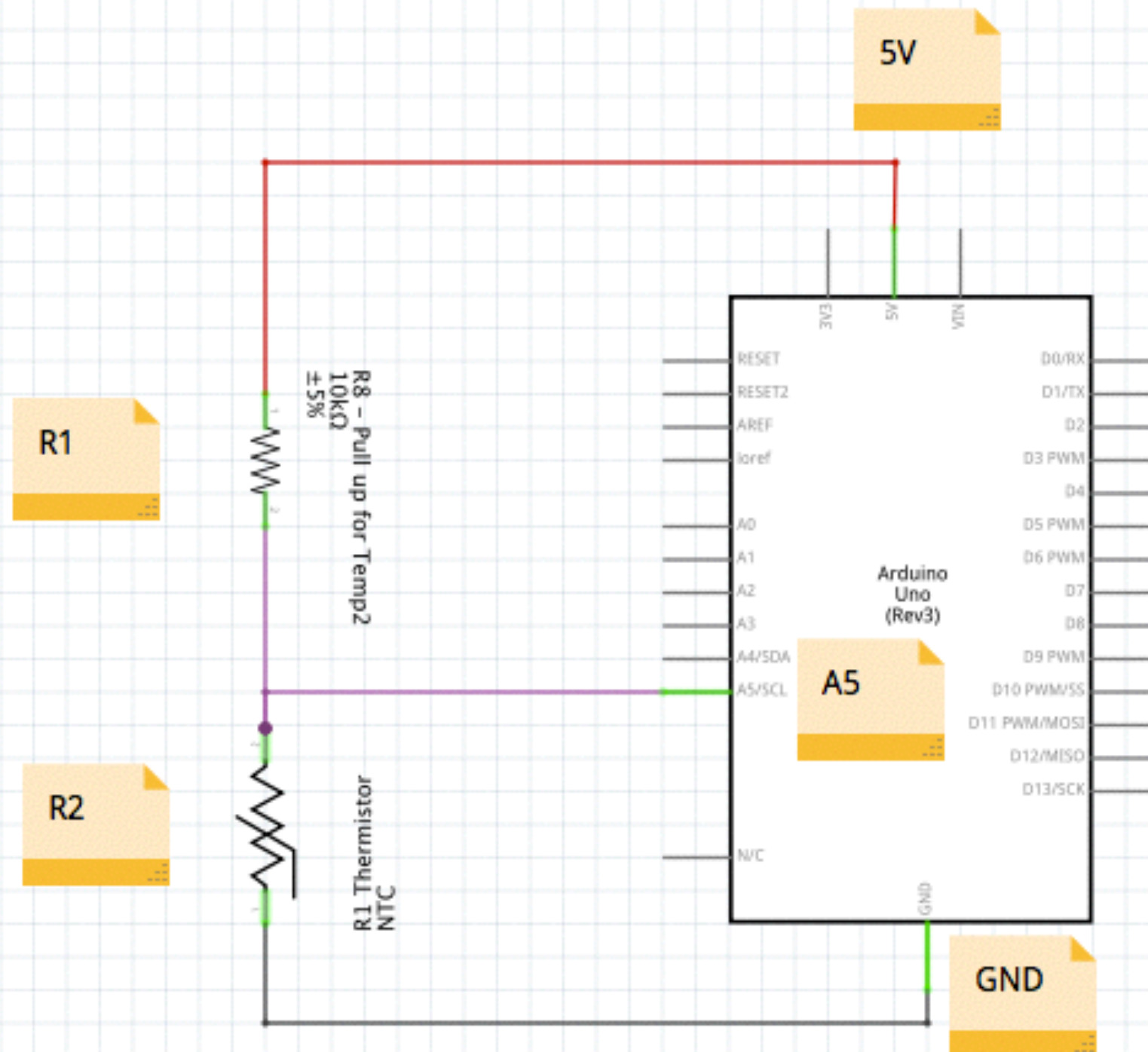
$$V_{out} = V_{in} \left(\frac{R_2}{R_1 + R_2} \right)$$





Selecting a heat source

- Lamp
 - Heat as a by product
- Microwave
 - Needs liquid to heat
- Infrared
 - 100W infrared
- Power resistor

$$P = \frac{I^2}{R}$$


$$7W = \frac{(12V)^2}{R}$$

$$R = \frac{144}{7} \approx 20 \Omega$$






Controlling the lamp

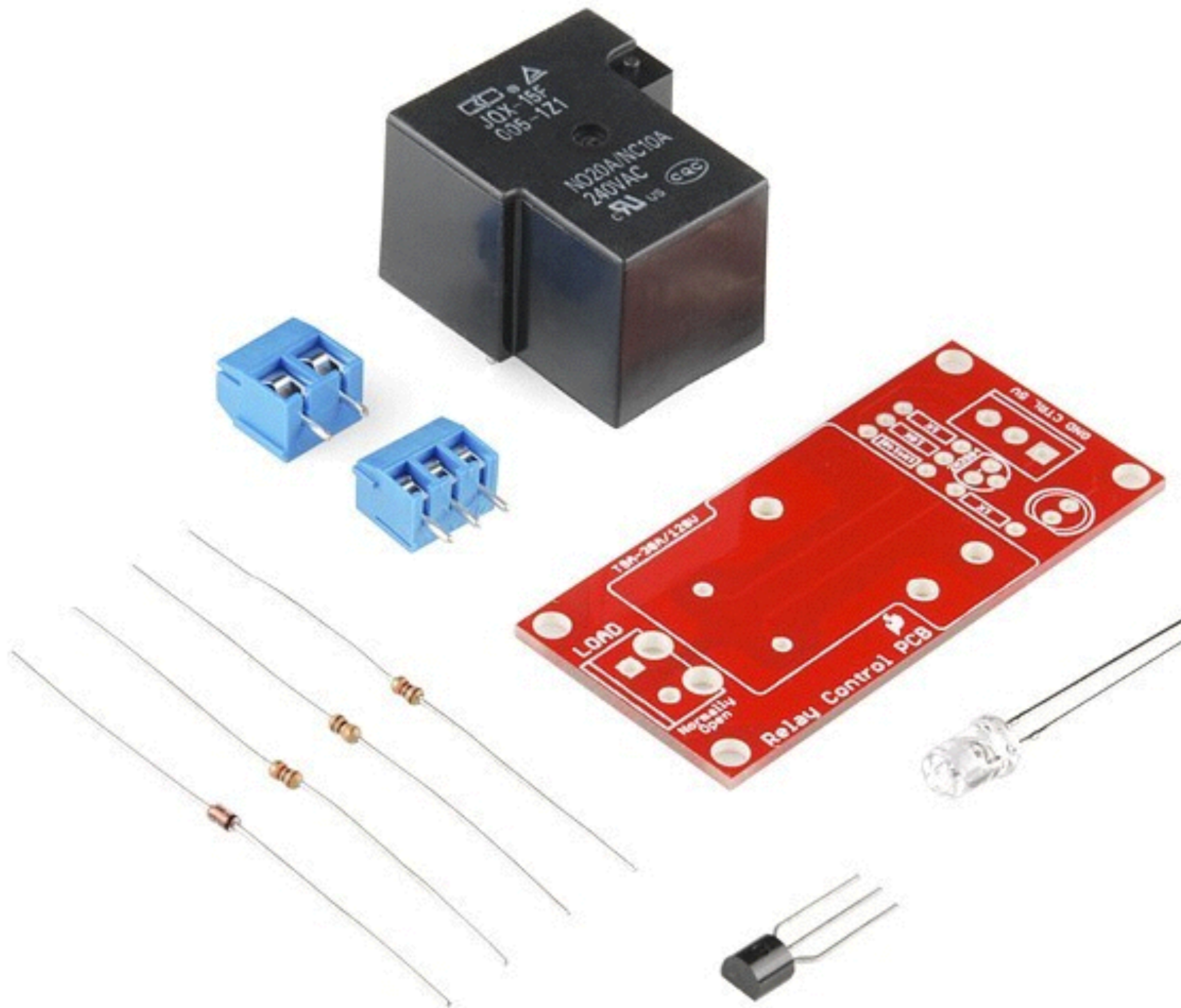



Relay schematic

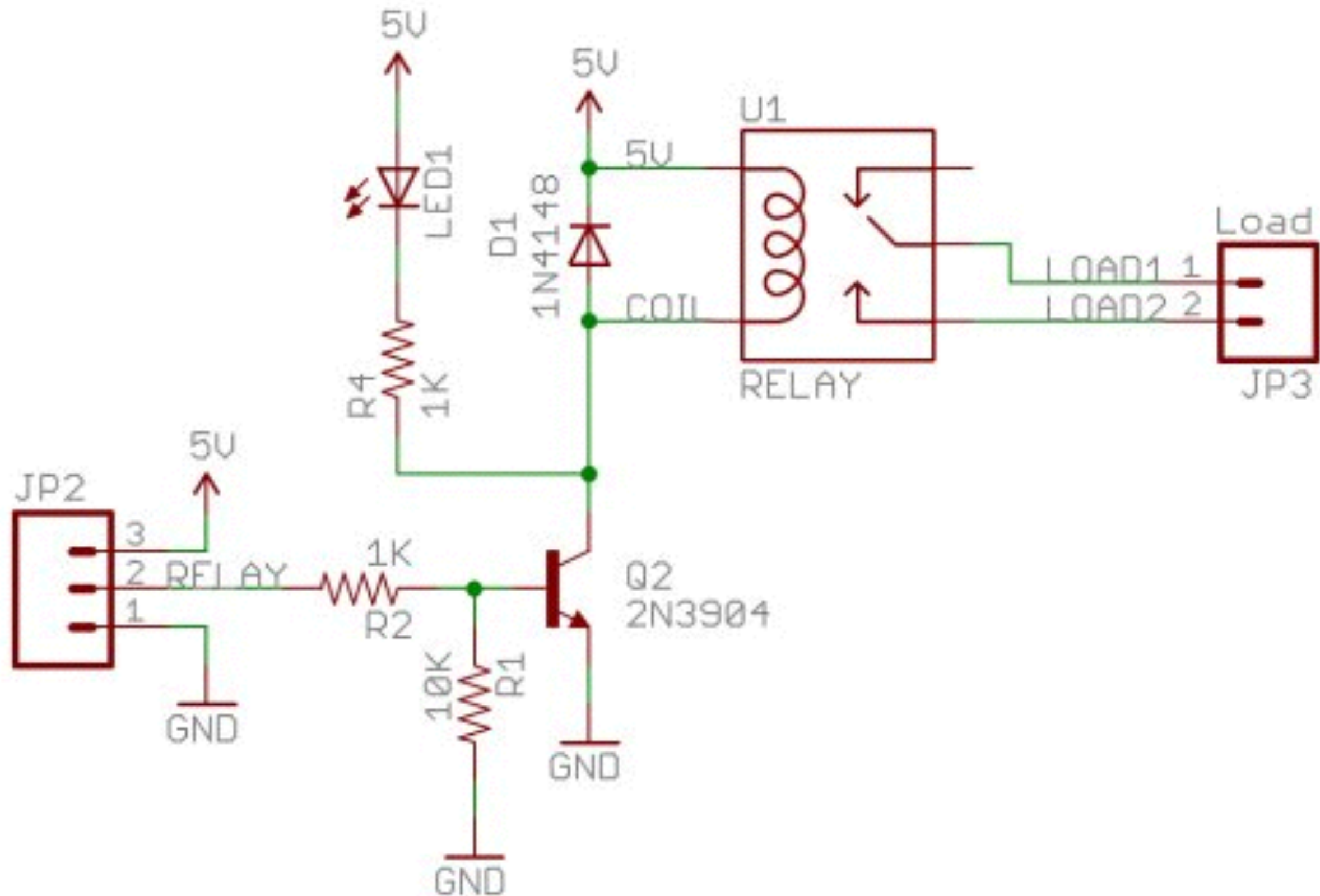




Push buttons

Pull down resistors


- 10 K Ohm

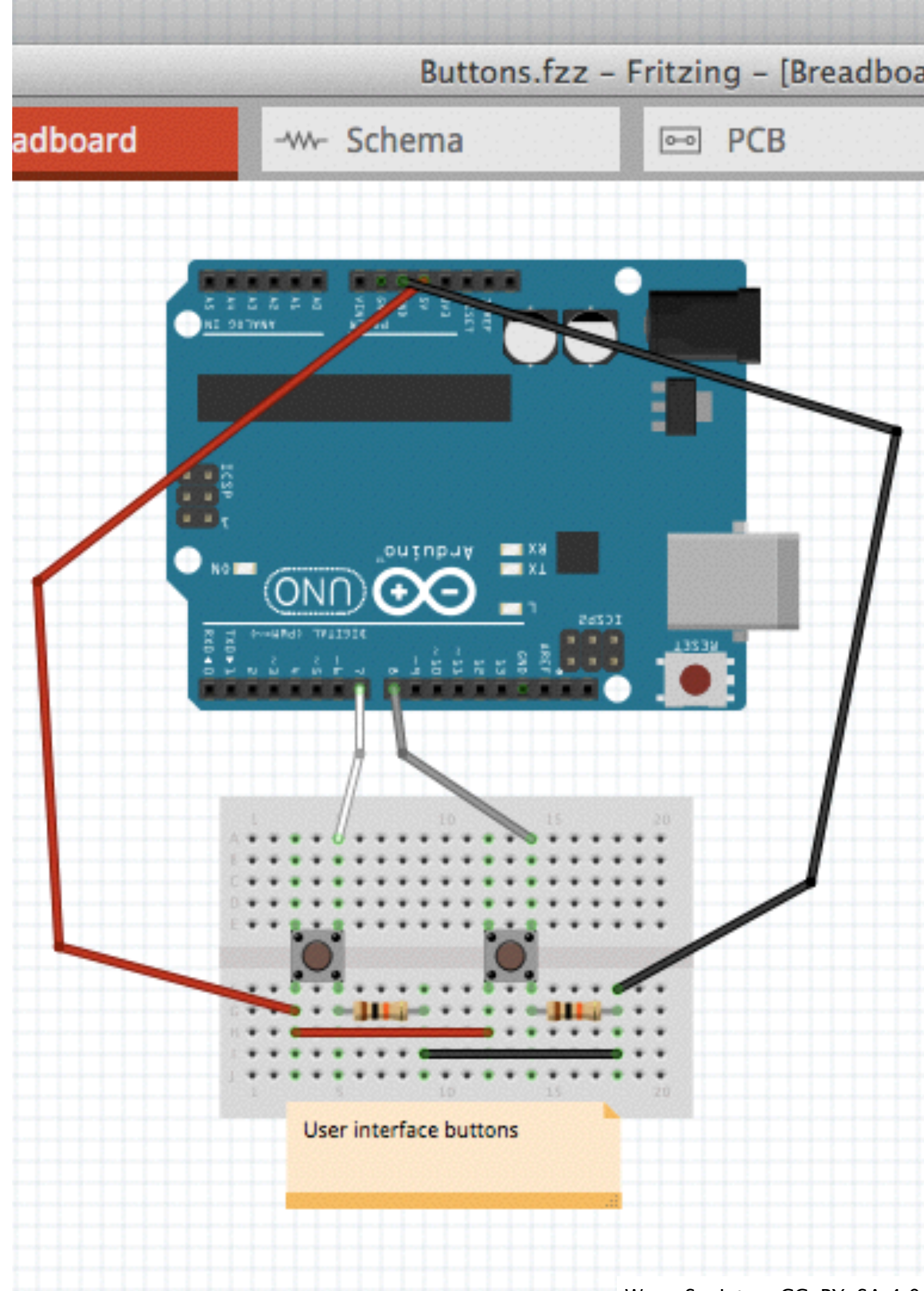




Fan speed controller

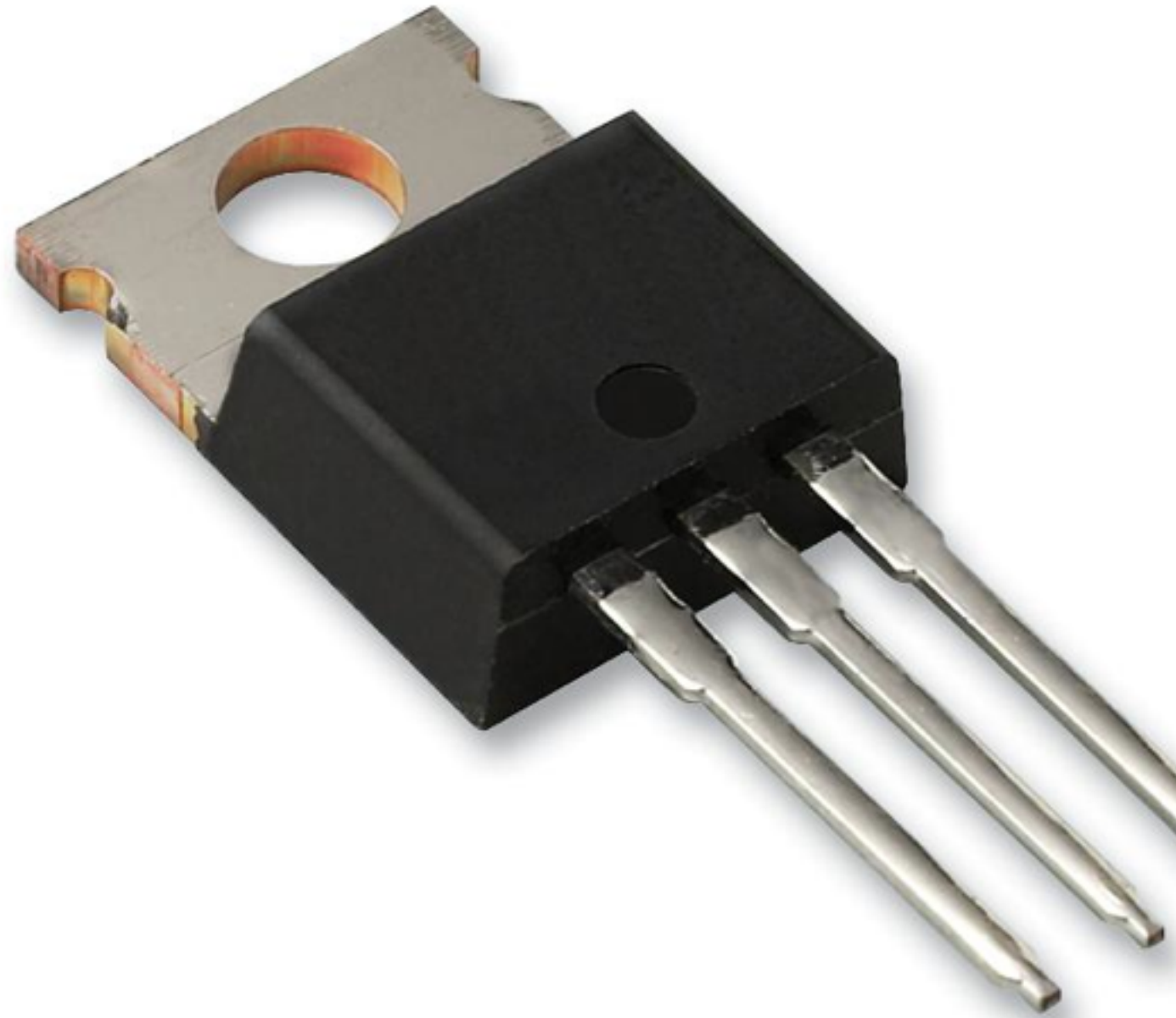- MOSFET
 - Semiconductor
- N-channel
- 60V
- 30A






Controlling the fan

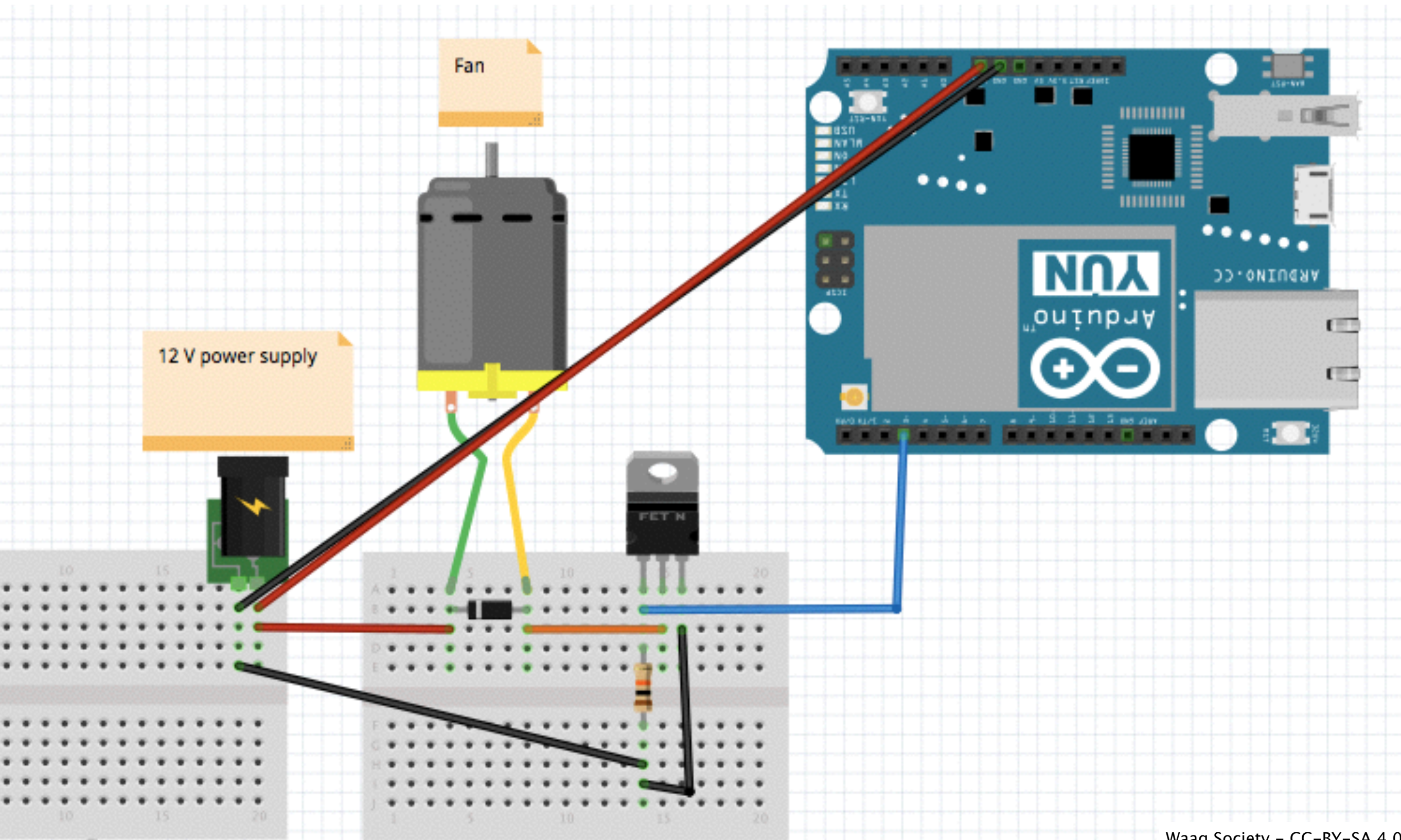




All of the electronics together

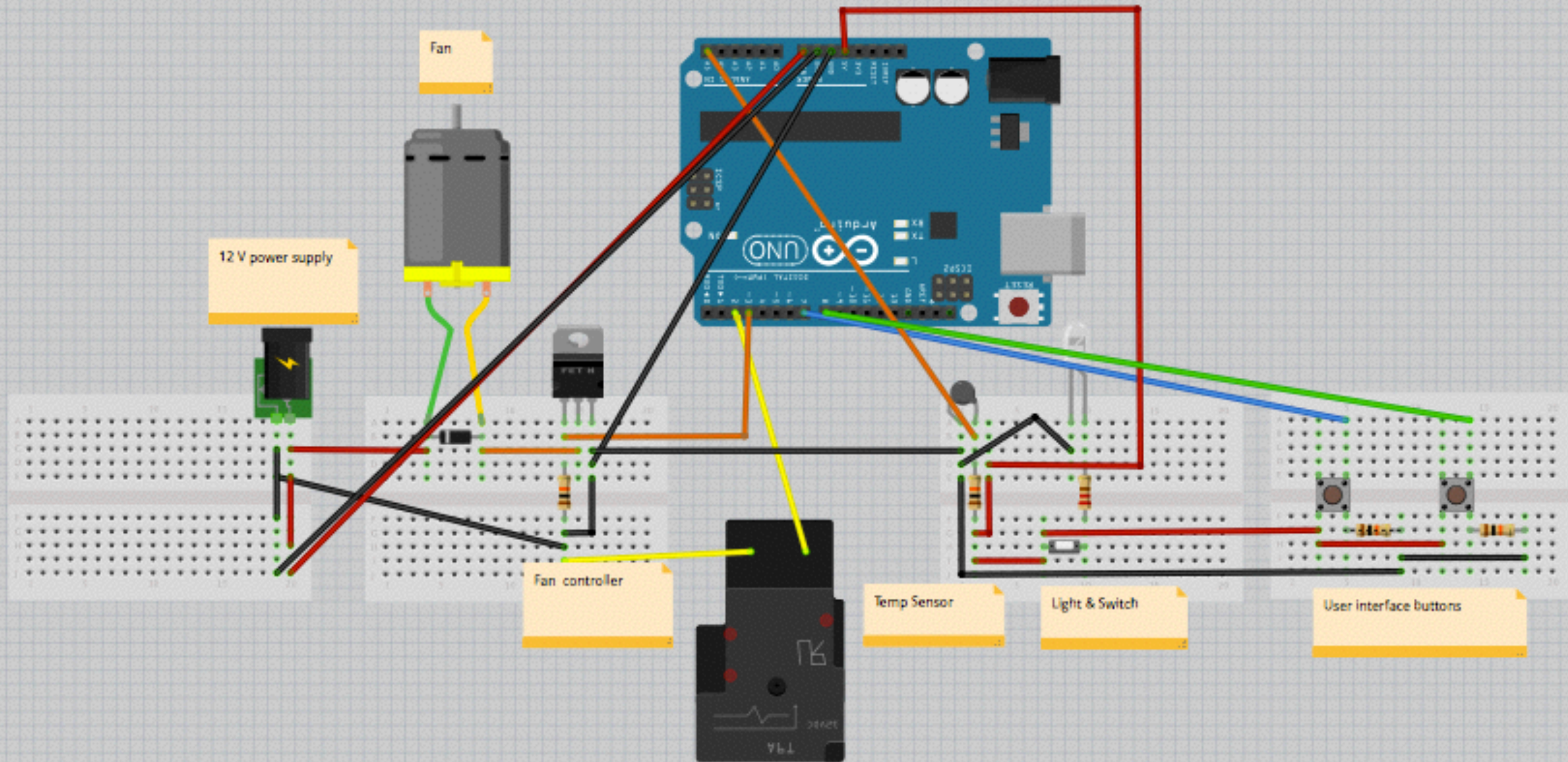



Schematic

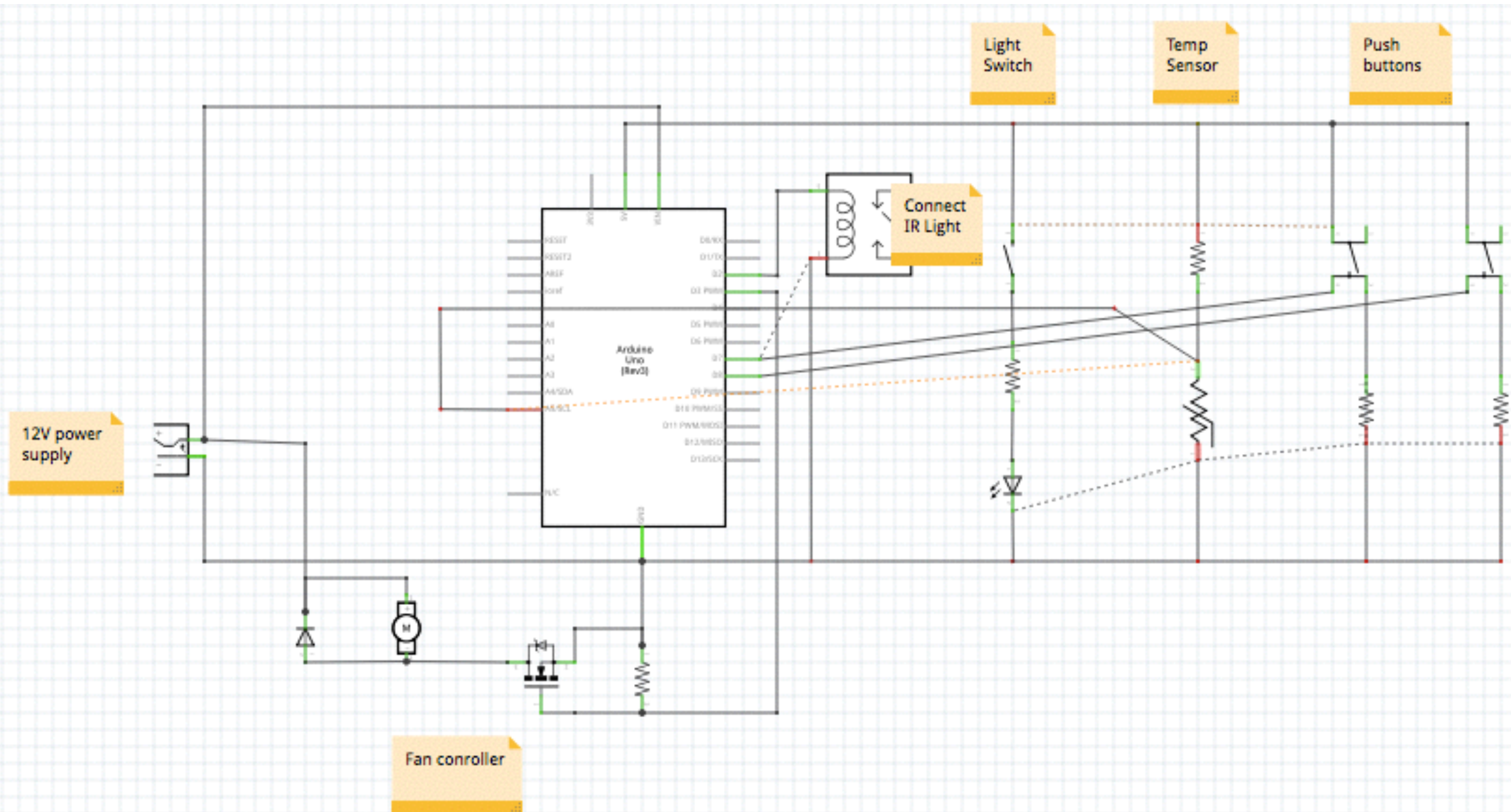



Power Supply

$$P = A \times I$$

$$\text{Power} = \text{Current} \times \text{Potential}$$

$$\text{Watt} = \text{Ampere} \times \text{Volt}$$

- 5 x 30 mA LEDs
- 1 x 250 mA Arduino
- 1 x 400 mA Fan
- 1 x 30 mA 7 segment display
- Total: 830 mA
- So a 1 Amp power supply should be enough





Arduino tutorial codes

- MOSFET code:
 - <http://bildr.org/2012/03/rfp30n06le-arduino/>
- 4 digit 7 segment:
 - http://dlnmh9ip6v2uc.cloudfront.net/datasheets/Components/LED/_7Seg_Example.pde
- Button code:
 - <http://arduino.cc/en/tutorial/button>
- Thermistor code:
 - <http://computers.tutsplus.com/tutorials/how-to-read-temperatures-with-arduino--mac-53714>



Code logic

- Measure temperature
 - Turn lamp on when temperature is lower than target
 - Turn lamp off when temperature is higher than target
- Check whether a button is pushed
 - If left button is pushed increase target temperature
 - If right button is pushed decrease target temperature
- Display current temperature
 - In case left or right button is pushed, display target temperature for 5 seconds




Nice to haves

- PID control
- Magnetic door lock
- Lever switch that checks whether door is locked
- Sound alarm in case door is open for too long
- Webcam inside



PID control

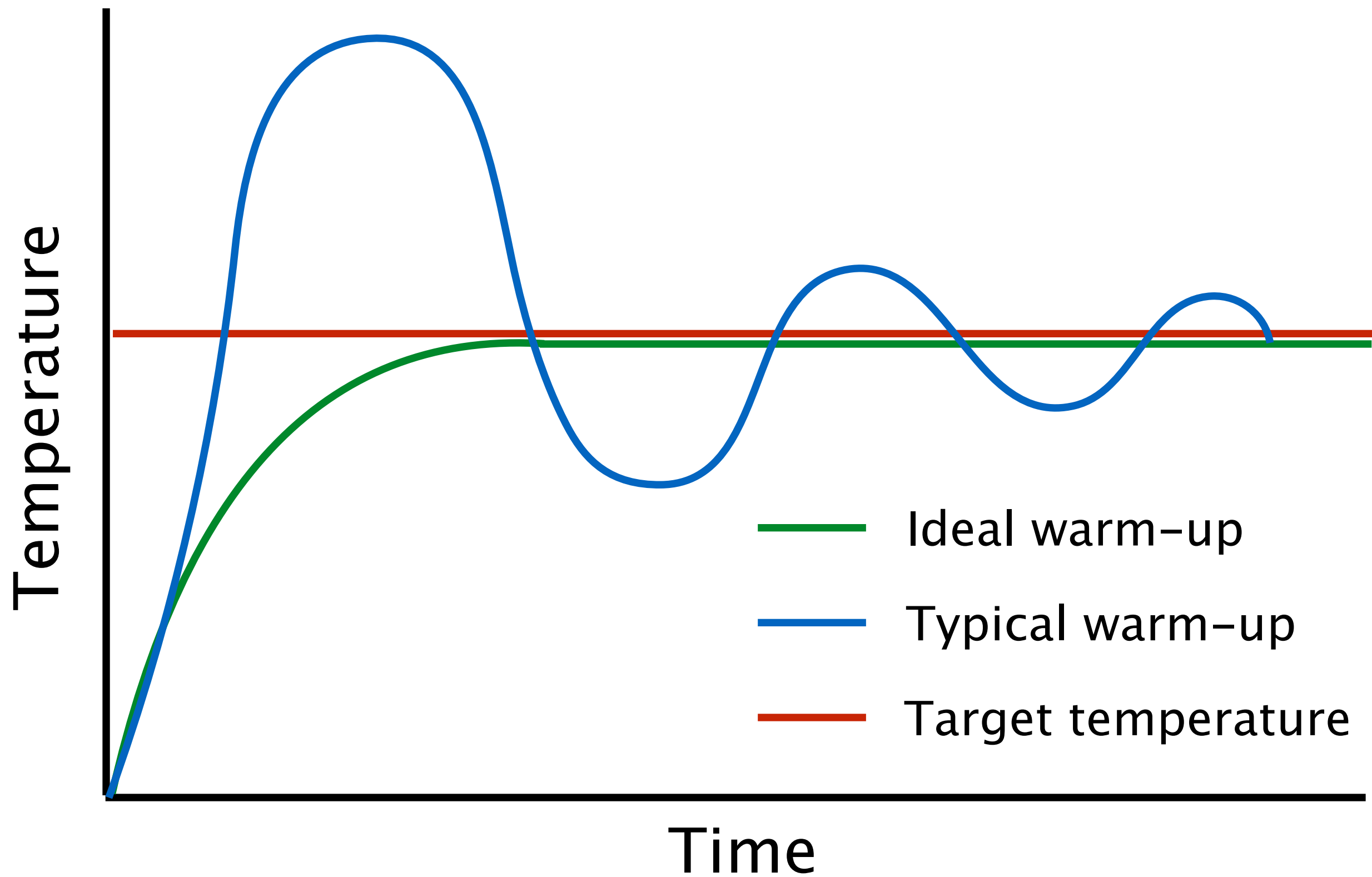



**some
rights
reserved**

These slides are published by Waag
Society under CC-BY-SA 4.0 license